

CS330 Architecture and Organization
Assignment Chapter 4

Your Name Here

Problem 1 — (Sections 4.1 and 4.4) Consider the following instruction:

Instruction: AND Rd, Rs, Rt

Interpretation: $\text{Reg}[\text{Rd}] = \text{Reg}[\text{Rs}] \text{ AND } \text{Reg}[\text{Rt}]$

- (a) (3 points) What are the values of control signals (RegWrite, ALU operation, MemRead, MemWrite, Branch) generated by the control unit in Figure 4.2 on p. 247 for the above instruction?
- (b) (3 points) Which resources (blocks) perform a useful function for this instruction?
- (c) (3 points) Which resources (blocks) produce outputs, but their outputs are not used for this instruction? Which resources produce no outputs for this instruction?

Answer:

- (a) RegWrite=1, since this writes a register
ALU operation=0000, since this is an AND instruction (see p. 259)
MemRead=0, since we don't read from Data memory
MemWrite=0, since we don't write to Data memory
Branch=0, since we don't branch
- (b) Instruction memory provides the instruction
Register file provides the arguments and destination
ALU performs the operation
PC+4 updates the program counter
- (c) Offset ALU produces an unused output
Data memory produces no output

Problem 2 — (Section 4.1) The basic single-cycle MIPS implementation in Figure 4.2 can only implement some instructions. New instructions can be added to an existing Instruction Set Architecture (ISA), but the decision whether or not to do that depends, among other things, on the cost and complexity the proposed addition introduces into the processor datapath and control. Consider the new instruction (that uses registers Rs and Rd) for both the base address and offset to load a word from data memory:

Instruction LWI Rt, Rd(Rs)

Interpretation: $\text{Reg}[\text{Rt}] = \text{Mem}[\text{Reg}[\text{Rd}] + \text{Reg}[\text{Rs}]]$

- (a) (2 points) Is this an R-type, I-type, J-type instruction, or do we need to invent a new instruction type to implement LWI?
- (b) (3 points) Which existing blocks (if any) can be used for this instruction?
- (c) (3 points) Which new functional blocks (if any) do we need for this instruction?
- (d) (5 points) What are the values of control signals (RegWrite, ALU operation, MemRead, MemWrite, Branch) generated by the control unit in Figure 4.2? What new signals do we need (if any) from the control unit to support this instruction?

Answer:

- (a) This is an R-type instruction
- (b) Instruction memory
Register file
ALU
Data memory
- (c) We don't need any new blocks
- (d) RegWrite=1, since this writes a register
ALU operation=0010, since this contains an ADD operation (see p. 259)
MemRead=1, since we read from Data memory
MemWrite=0, since we don't write to Data memory
Branch=0, since we don't branch

Problem 3 — (Section 4.3) Refer to Figure 4.11 on p. 258 of the text. In your answers to these questions, refer to the parts of the processor by these names:

- Instruction memory
- Data memory
- Register file
- Sign extend unit
- Shift-left 2 unit
- ALU (the full-capability ALU located between the Register file and Data memory)
- Add PC+4 (located in upper-left of diagram)
- Add PC offset (located in upper-right of diagram)

Determine which parts of the processor are used when executing the following instructions.

- (a) (4 points) add \$t0, \$t1, \$t2
- (b) (4 points) addi \$s0, \$s1, -1
- (c) (4 points) beq \$sp, \$gp, label0 (Assume the branch does **not** take place.)
- (d) (4 points) bne \$t0, \$t1, label1 (Assume the branch takes place.)
- (e) (4 points) sw \$t0, 1024(\$s0)

Answer:

- (a) (4 points) add \$t0, \$t1, \$t2
Instruction memory
Register file
ALU
Add PC+4 unit
- (b) (4 points) addi \$s0, \$s1, -1
Instruction memory
Register file
Sign extend unit

ALU
Add PC+4 unit

- (c) (4 points) `beq $sp, $gp, label0` (Assume the branch does **not** take place.)

Instruction memory
Register file
ALU
Add PC+4 unit

- (d) (4 points) `bne $t0, $t1, label1` (Assume the branch takes place.)

Instruction memory
Register file
ALU Sign extend unit
Shift-left 2 unit
Add PC offset unit

- (e) (4 points) `sw $t0, 1024($s0)`

Instruction memory
Register file
Sign extend unit
ALU
Data memory
Add PC+4 unit

Problem 4 — (Section 4.3) Suppose the processor is performing the instruction `add $t0, $t1, $t2`.

1. (2 points) Which input should the `ALUSrc` mux select: Read data 2, Sign extension unit, or is this a don't care?
2. (2 points) Which input should the `MemtoReg` mux select: Read data, ALU Result, or is this a don't care?
3. (2 points) Which input should the `PCSrc` mux select: Add PC+4, Add PC offset, or is this a don't care?

Answer:

- (a) Read data 2
(b) ALU result
(c) Add PC+4

Problem 5 — (Section 4.3) Suppose the processor is performing the instruction `lw $t0, -4($s0)`.

1. (2 points) Which input should the `ALUSrc` mux select: Read data 2, Sign extension unit, or is this a don't care?
2. (2 points) Which input should the `MemtoReg` mux select: Read data, ALU Result, or is this a don't care?
3. (2 points) Which input should the `PCSrc` mux select: Add PC+4, Add PC offset, or is this a don't care?

Answer:

- (a) Sign extension unit
- (b) Read data
- (c) Add PC+4

Problem 6 — (Section 4.3) Suppose the processor is performing the instruction `bne $a0, $zero, loop`.

1. (2 points) Which input should the `ALUSrc` mux select: Read data 2, Sign extension unit, or is this a don't care?
2. (2 points) Which input should the `MemtoReg` mux select: Read data, ALU Result, or is this a don't care?
3. (2 points) Which input should the `PCSrc` mux select: Add PC+4, Add PC offset, or is this a don't care?

Answer:

- (a) Read data 2
- (b) Don't care
- (c) Add PC offset